
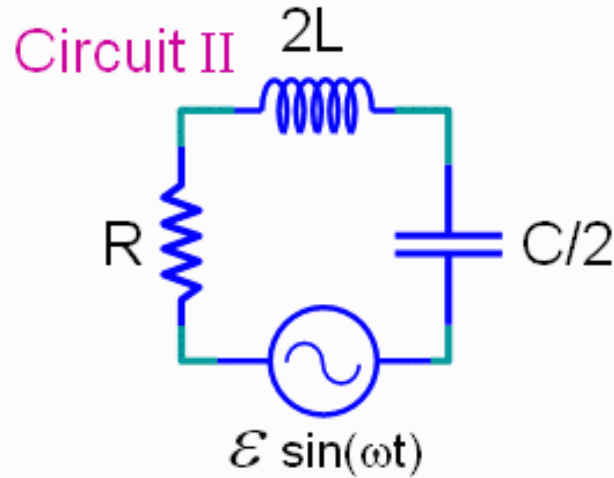


CheckPoint 1b

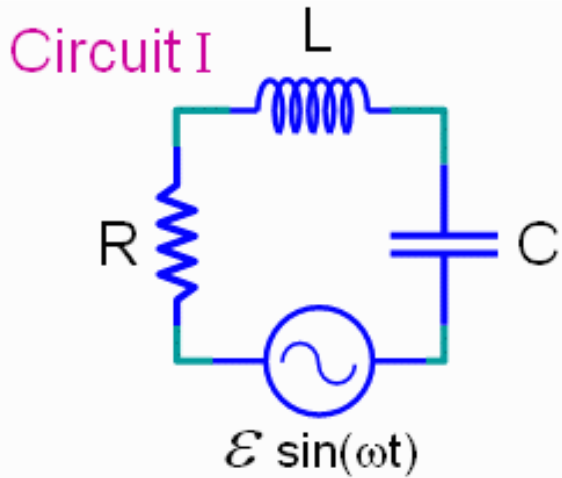

Consider two RLC circuits with identical generators and resistors. Both circuits are driven at the resonant frequency. Circuit II has twice the inductance and 1/2 the capacitance of circuit I as shown

Compare the peak voltage across the inductor in the two circuits

A. $V_I > V_{II}$

B. $V_I = V_{II}$

C. $V_I < V_{II}$

Voltage in second circuit will be twice that of the first because of the $2L$ compared to L .

Resonant Circuits: Question 3 (N = 813)

