

# Follow-Up from last lecture



Consider the harmonically driven series *LCR* circuit shown.


$$V_{max} = 100 \text{ V}$$

$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V} (= 80 \sqrt{2})$$

The current leads generator voltage by  $45^\circ$  ( $\cos = \sin = 1/\sqrt{2}$ )


*L* and *R* are unknown.

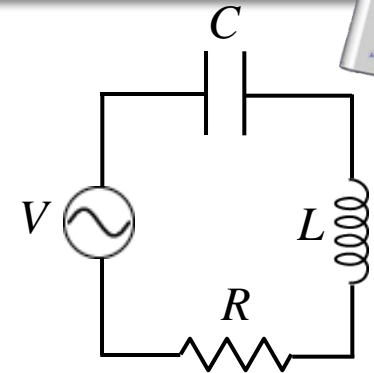

$$R = 25\sqrt{2} \text{ k}\Omega$$

$$X_L = 15\sqrt{2} \text{ k}\Omega$$

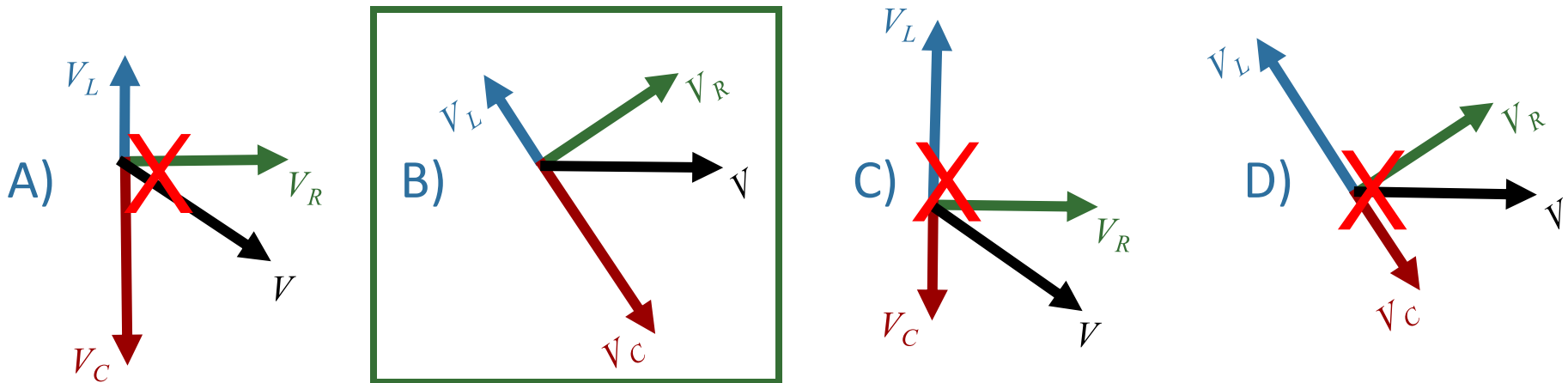What does the phasor diagram look like at  $t = 0$ ? (assume  $V = V_{max} \sin \omega t$ )



$V = V_{max} \sin \omega t \rightarrow V$  is horizontal at  $t = 0$  ( $V = 0$ )

$$\vec{V} = \vec{V}_L + \vec{V}_C + \vec{V}_R \quad \rightarrow \quad V_L < V_C \text{ if current leads generator voltage}$$