

Follow-Up from Last Lecture

Consider the harmonically driven series *LCR* circuit shown.


$$V_{max} = 100 \text{ V}$$

$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V} (= 80 \sqrt{2})$$

The current leads generator voltage by 45° ($\cos = \sin = 1/\sqrt{2}$)

L and *R* are unknown.

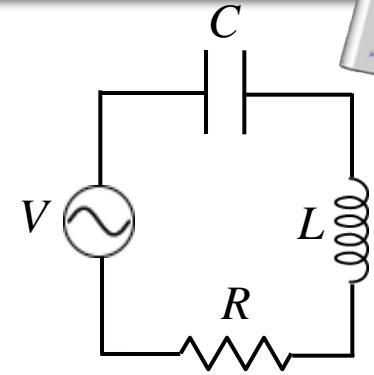


How should we change ω to bring circuit to resonance?

A) decrease ω


B) increase ω

C) Not enough info

Original ω

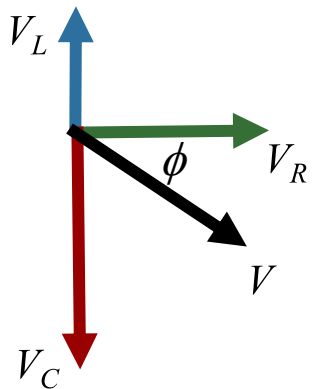

At resonance

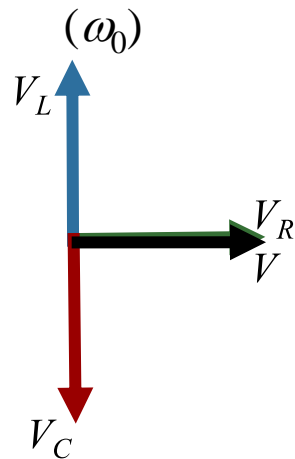

At resonance

$$X_L = X_C$$

X_L increases

X_C decreases

→ ω increases