

More Follow-Up



Consider the harmonically driven series *LCR* circuit shown.

$$V_{max} = 100 \text{ V}$$


$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V} (= 80 \sqrt{2})$$

$$\longrightarrow X_C = 40\sqrt{2} \text{ k}\Omega$$

The current leads generator voltage by 45° ($\cos = \sin = 1/\sqrt{2}$)

L and *R* are unknown.

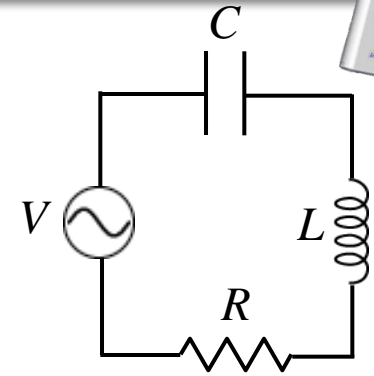

$$R = 25\sqrt{2} \text{ k}\Omega$$

$$X_L = 15\sqrt{2} \text{ k}\Omega$$

By what factor should we increase ω to bring circuit to resonance?

i.e. if $\omega_0 = f\omega$, what is f ?

A) $f = \sqrt{2}$

B) $f = 2\sqrt{2}$

C) $f = \sqrt{\frac{8}{3}}$

D) $f = \sqrt{\frac{8}{5}}$

If ω is increased by a factor of f :

X_L increases by factor of f

X_C decreases by factor of f



$$X_L \rightarrow f \cdot 15\sqrt{2}$$

$$X_C \rightarrow (1/f) \cdot 40\sqrt{2}$$

At resonance

$$X_L = X_C$$

$$\longrightarrow 15f = \frac{40}{f} \longrightarrow f^2 = \frac{40}{15}$$

$$\longrightarrow f = \sqrt{\frac{8}{3}}$$