

Current Follow-Up

Consider the harmonically driven series *LCR* circuit shown.

$$V_{max} = 100 \text{ V}$$


$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V} (= 80 \sqrt{2})$$

The current leads generator voltage by 45° ($\cos = \sin = 1/\sqrt{2}$)

L and *R* are unknown.

What is the maximum current at resonance

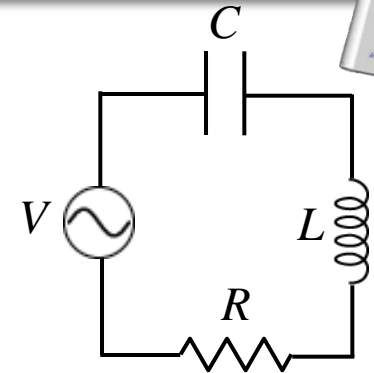

$$R = 25\sqrt{2} \text{ k}\Omega$$

$$X_L = 15\sqrt{2} \text{ k}\Omega$$

$$\omega_0 = \sqrt{\frac{8}{3}} \omega$$

A) $I_{max}(\omega_0) = \sqrt{2} \text{ mA}$

B) $I_{max}(\omega_0) = 2\sqrt{2} \text{ mA}$

C) $I_{max}(\omega_0) = \sqrt{\frac{8}{3}} \text{ mA}$

At resonance $X_L = X_C \rightarrow Z = R \rightarrow I_{max}(\omega_0) = \frac{V_{max}}{R} = \frac{100}{25\sqrt{2}} = 2\sqrt{2} \text{ mA}$