## Follow-Up

Switch *S* has been open a long time when at t = 0, it is closed. Capacitor *C* has circular plates of radius *R*. At time  $t = t_1$ , a current  $I_1$  flows in the circuit and the capacitor carries charge  $Q_1$ .

What is the time dependence of the magnetic field B at a radius r between the plates of the capacitor?







*B* at fixed *r* is proportional to the current *I* Close switch:  $V_C = 0 \Rightarrow I = V/R_a$  (maximum) *I* exponentially decays with time constant  $\tau = R_a C$