
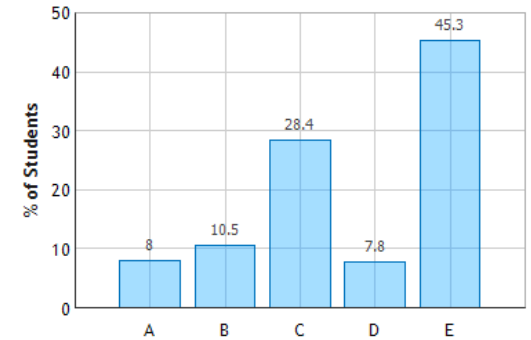


Checkpoint 3

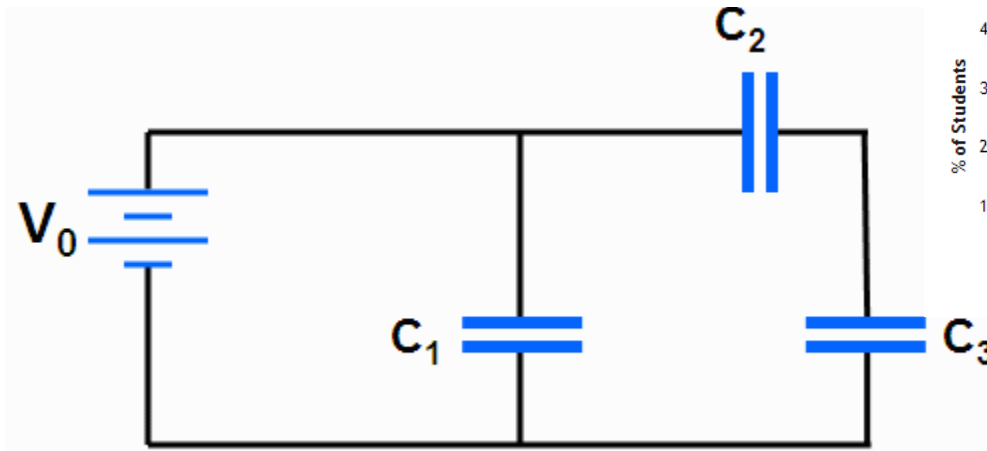

A circuit consists of three unequal capacitors C_1 , C_2 , and C_3 which are connected to a battery of voltage V_0 . The capacitance of C_2 is twice that of C_1 . The capacitance of C_3 is three times that of C_1 . The capacitors obtain charges Q_1 , Q_2 , and Q_3 .



~~A.~~ $Q_1 > Q_3 > Q_2$ ~~B.~~ $Q_1 > Q_2 > Q_3$ **C.** $Q_1 > Q_2 = Q_3$ **D.** $Q_1 = Q_2 = Q_3$ **E.** $Q_1 < Q_2 = Q_3$

1. See immediately: $Q_2 = Q_3$ (capacitors in series)

2. How about Q_1 vs. Q_2 and Q_3 ? Calculate C_{23} first.

$$\frac{1}{C_{23}} = \frac{1}{C_2} + \frac{1}{C_3} = \frac{1}{2C_1} + \frac{1}{3C_1} = \frac{5}{6C_1}$$



$$C_{23} = \frac{6}{5}C_1$$



$$Q_1 = C_1 V_0$$

$$Q_{23} = Q_2 = Q_3 = C_{23} V_0 = \frac{6}{5} C_1 V_0$$