
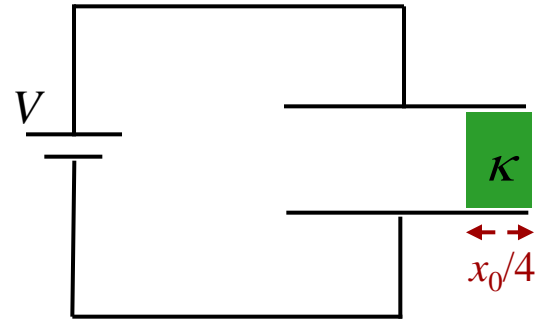


Calculation

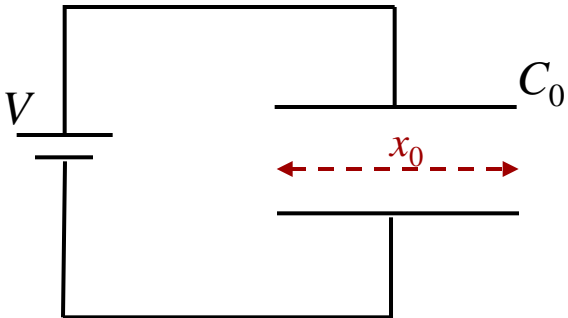


An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

What is Q_f , the final charge on the capacitor?

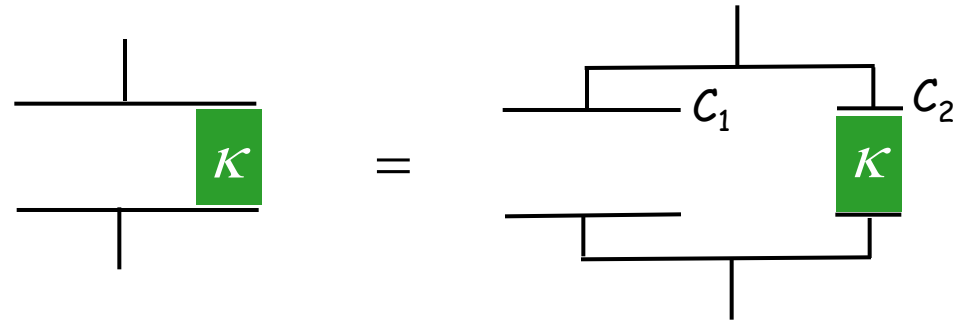Can consider capacitor to be two capacitances, C_1 and C_2 , in parallel



What is C_1 ?

- A) $C_1 = C_0$ B) $C_1 = \frac{3}{4}C_0$ C) $C_1 = \frac{4}{3}C_0$ D) $C_1 = \frac{1}{4}C_0$

In general. For parallel plate capacitor: $C = \epsilon_0 A/d$

$$\begin{matrix} A = \frac{3}{4}A_0 \\ d = d_0 \end{matrix} \quad \rightarrow \quad C_1 = \frac{3}{4}(\epsilon_0 A_0/d_0) \quad \rightarrow \quad C_1 = \frac{3}{4}C_0$$