
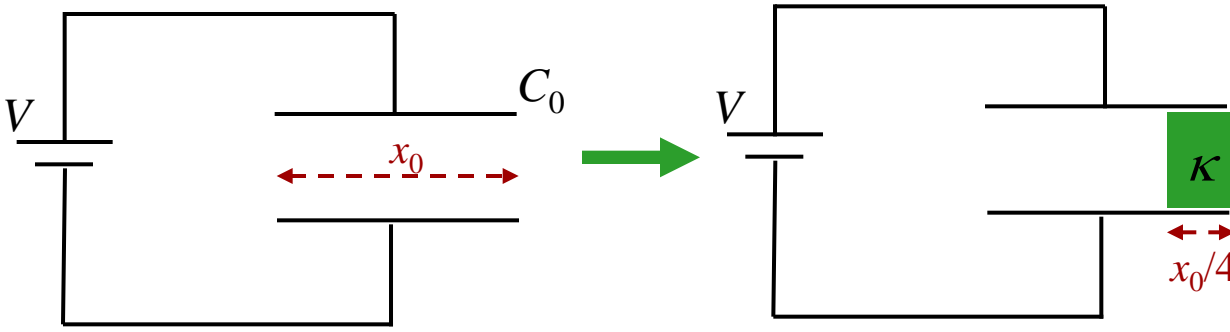


Calculation

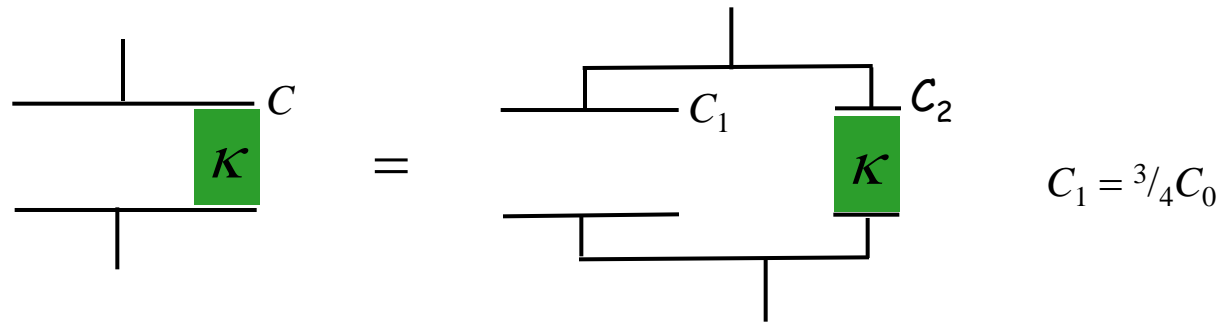

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.



What is Q_f , the final charge on the capacitor?

$$C_1 = \frac{3}{4}C_0$$

$$C_2 = \frac{1}{4} \kappa C_0$$

What is C ?

A) $C = C_1 + C_2$

B) $C = C_1 + \kappa C_2$

C) $C = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)^{-1}$

$C =$ parallel combination of C_1 and C_2 : $C = C_1 + C_2$

$\rightarrow C = C_0 \left(\frac{3}{4} + \frac{1}{4} \kappa \right)$