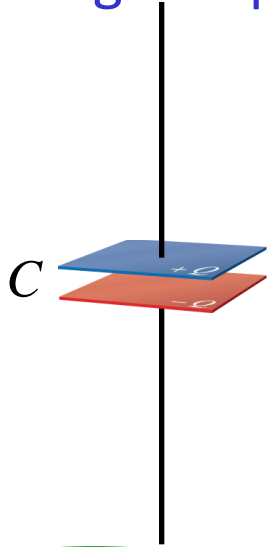


Checkpoint 2


Which has lowest total capacitance?

- A) Single Capacitor B) 4 Capacitors C) Same

:



$$C_{total} = C$$

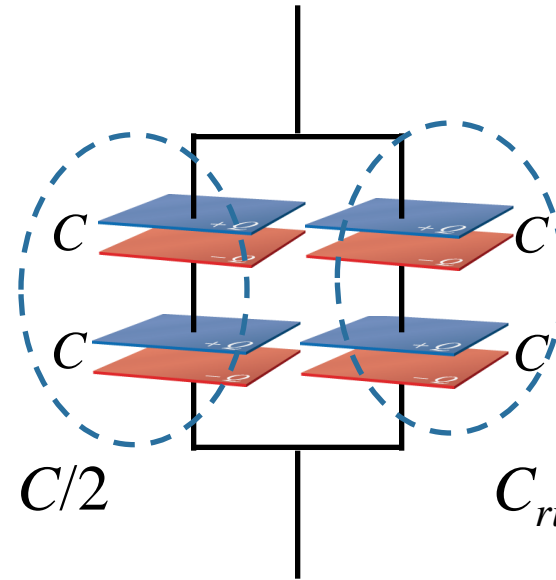

$$C_{total} = C_{left} + C_{right}$$

$$C_{total} = C$$

