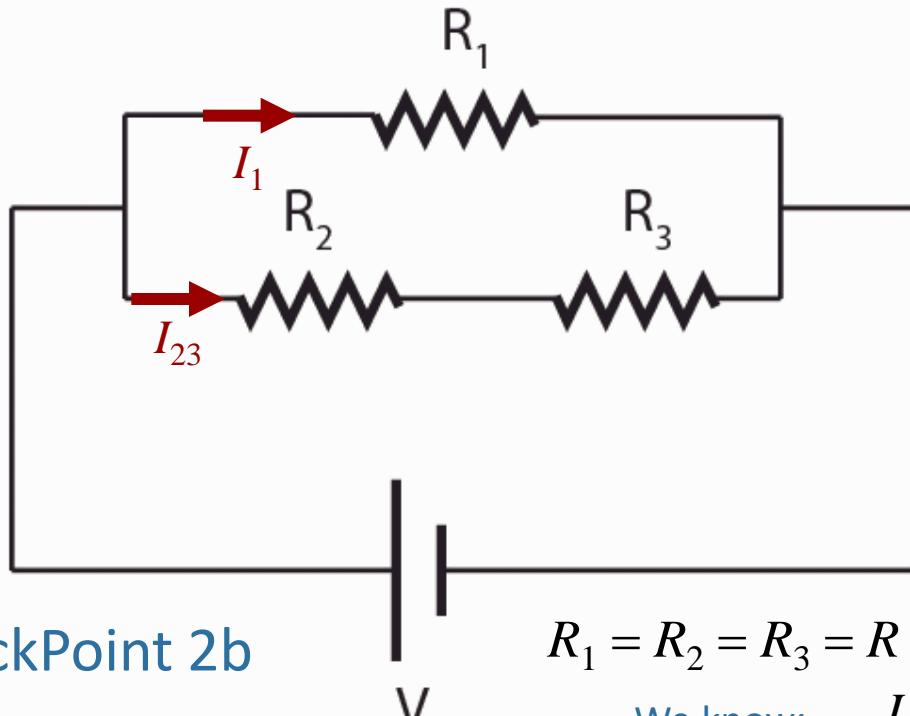


Checkpoint 2b



CheckPoint 2b

Compare the current through R_1
with the current through R_2

- A $I_1/I_2 = 1/2$
- B $I_1/I_2 = 1/3$
- C $I_1/I_2 = 1$
- D $I_1/I_2 = 2$
- E $I_1/I_2 = 3$

$$R_1 = R_2 = R_3 = R$$

We know:

$$I_{23} = \frac{V}{R_2 + R_3}$$

Similarly:

$$I_1 = \frac{V}{R_1}$$



$$I_1 = I_{23} \frac{R_2 + R_3}{R_1}$$



$$\frac{I_1}{I_{23}} = \frac{R_2 + R_3}{R_1} = 2$$

