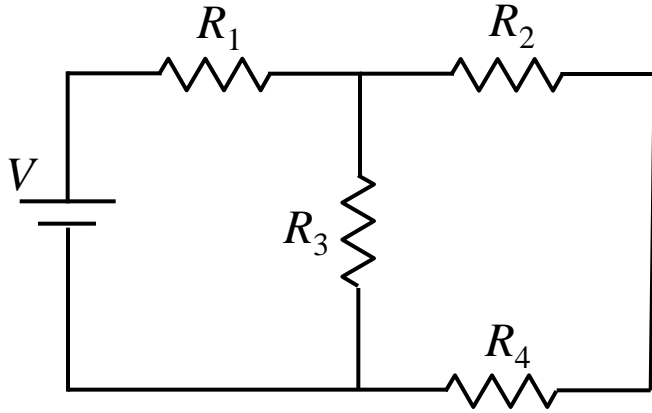


# Calculation



In the circuit shown:  $V = 18V$ ,  
 $R_1 = 1\Omega$ ,  $R_2 = 2\Omega$ ,  $R_3 = 3\Omega$ , and  $R_4 = 4\Omega$ .

What is  $V_2$ , the voltage across  $R_2$ ?

## Conceptual Analysis:

Ohm's Law: when current  $I$  flows through resistance  $R$ , the potential drop  $V$  is given by:  
 $V = IR$ .

Resistances are combined in series and parallel combinations

$$R_{series} = R_a + R_b$$

$$(1/R_{parallel}) = (1/R_a) + (1/R_b)$$

## Strategic Analysis:

Combine resistances to form equivalent resistances

Evaluate voltages or currents from Ohm's Law

Expand circuit back using knowledge of voltages and currents