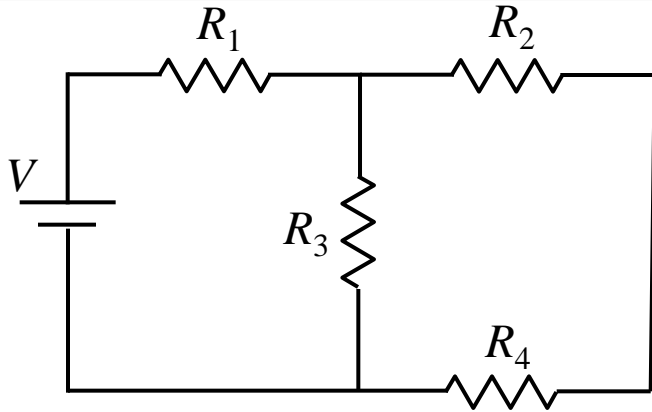


Calculation



In the circuit shown: $V = 18V$,
 $R_1 = 1\Omega$, $R_2 = 2\Omega$, $R_3 = 3\Omega$, and $R_4 = 4\Omega$.

What is V_2 , the voltage across R_2 ?


Combine Resistances:

R_1 and R_2 are connected:


A) in series

B) in parallel

C) neither in series nor in parallel

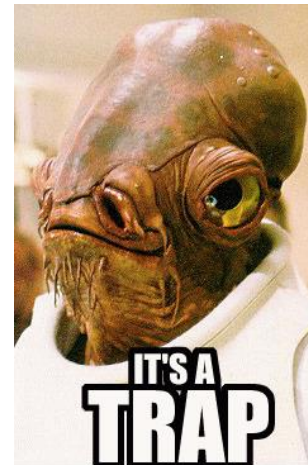

Parallel Combination

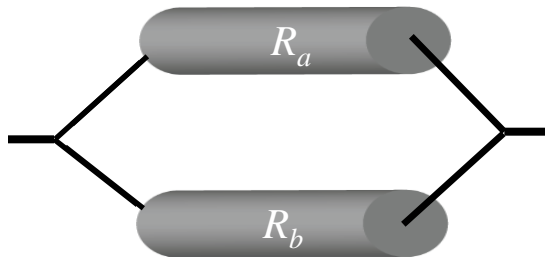

Parallel: Can make a loop that contains only those two resistors

Series Combination



Series : Every loop with resistor 1 also has resistor 2.