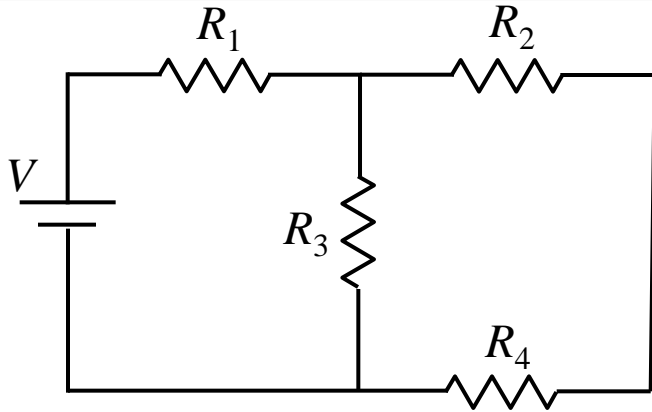


Calculation




In the circuit shown: $V = 18V$,
 $R_1 = 1\Omega$, $R_2 = 2\Omega$, $R_3 = 3\Omega$, and $R_4 = 4\Omega$.


What is V_2 , the voltage across R_2 ?

R_2 and R_4 are connected in series (R_{24}) which is connected in parallel with R_3

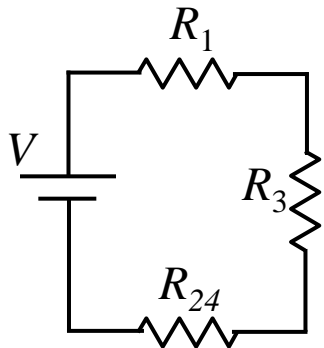
Redraw the circuit using the equivalent resistor $R_{24} =$ series combination of R_2 and R_4 .



(A)

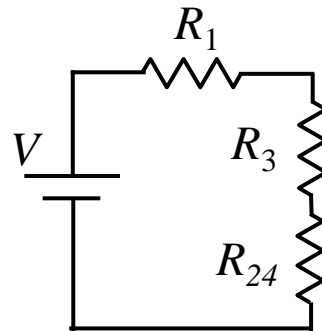

(B)

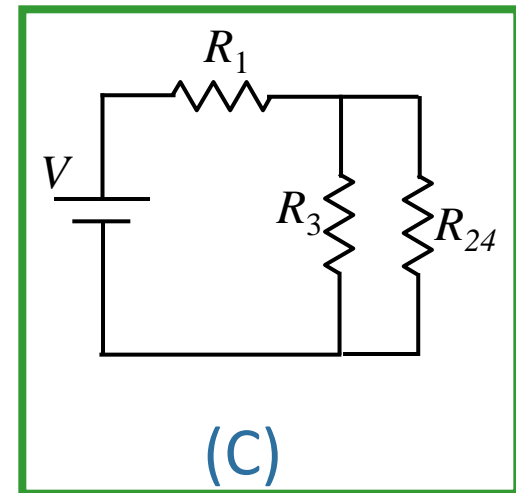

(C)