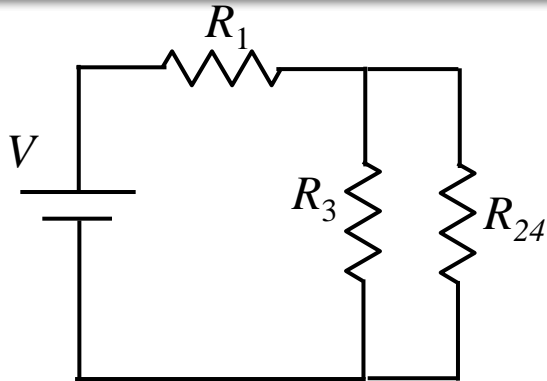


Calculation



In the circuit shown: $V = 18V$,
 $R_1 = 1\Omega$, $R_2 = 2\Omega$, $R_3 = 3\Omega$, and $R_4 = 4\Omega$.

What is V_2 , the voltage across R_2 ?

Combine Resistances:

R_2 and R_4 are connected in series = R_{24}
 R_3 and R_{24} are connected in parallel = R_{234}

What is the value of R_{234} ?

A) $R_{234} = 1 \Omega$ B) $R_{234} = 2 \Omega$ C) $R_{234} = 4 \Omega$ D) $R_{234} = 6 \Omega$

R_2 and R_4 in series \rightarrow $R_{24} = R_2 + R_4 = 2\Omega + 4\Omega = 6\Omega$

$(1/R_{parallel}) = (1/R_a) + (1/R_b)$ \rightarrow $1/R_{234} = (1/3) + (1/6) = (3/6) \Omega^{-1}$ \rightarrow $R_{234} = 2 \Omega$