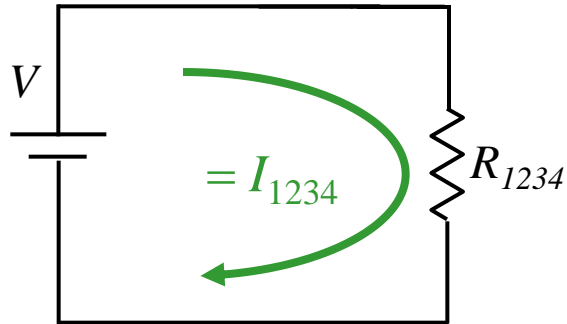



Calculation



In the circuit shown: $V = 18V$,
 $R_1 = 1\Omega$, $R_2 = 2\Omega$, $R_3 = 3\Omega$, and $R_4 = 4\Omega$.

$$R_{24} = 6\Omega \quad R_{234} = 2\Omega \quad I_{1234} = 6A$$

What is V_2 , the voltage across R_2 ?

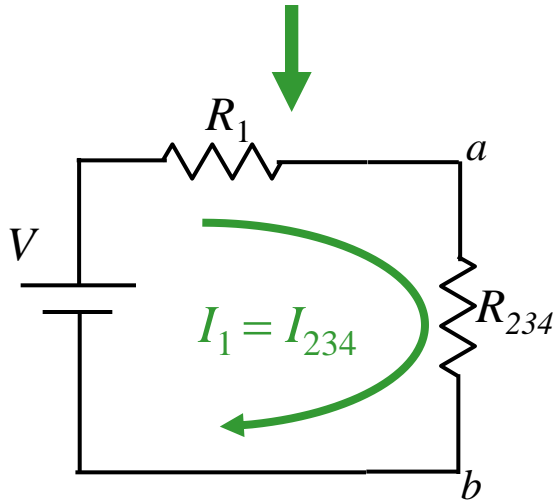

$$I_{234} = I_{1234} \quad \text{Since } R_1 \text{ in series with } R_{234}$$

$$\begin{aligned} V_{234} &= I_{234} R_{234} \\ &= 6 \times 2 \\ &= 12 \text{ Volts} \end{aligned}$$

What is V_{ab} , the voltage across R_{234} ?

A) $V_{ab} = 1V$

B) $V_{ab} = 2V$

C) $V_{ab} = 9V$

D) $V_{ab} = 12V$

E) $V_{ab} = 16V$