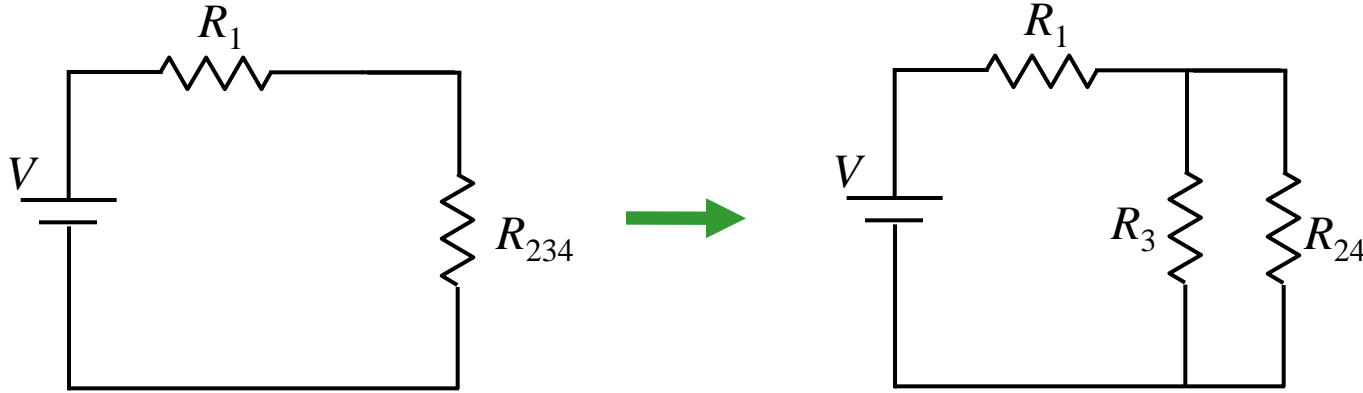


Calculation



$V = 18V$
 $R_1 = 1\Omega$
 $R_2 = 2\Omega$
 $R_3 = 3\Omega$
 $R_4 = 4\Omega$
 $R_{24} = 6\Omega$
 $R_{234} = 2\Omega$
 $I_{1234} = 6 \text{ Amps}$
 $I_{234} = 6 \text{ Amps}$
 $V_{234} = 12V$
What is V_2 ?

Which of the following are true?

A) $V_{234} = V_{24}$

B) $I_{234} = I_{24}$

C) Both A+B

D) None

R_3 and R_{24} were combined in parallel to get R_{234} → Voltages are same!

Ohm's Law

$$\begin{aligned} I_{24} &= V_{24} / R_{24} \\ &= 12 / 6 \\ &= 2 \text{ Amps} \end{aligned}$$