
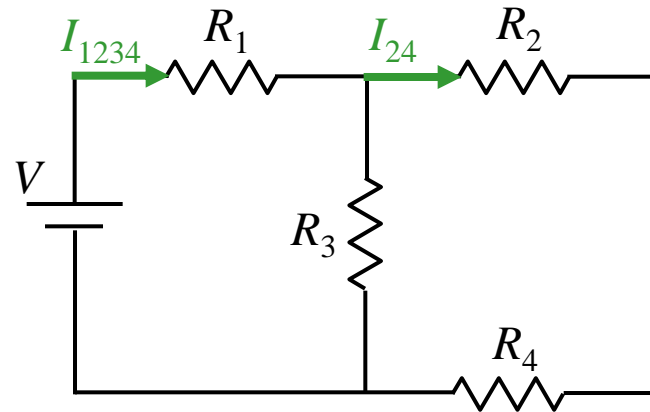


Calculation

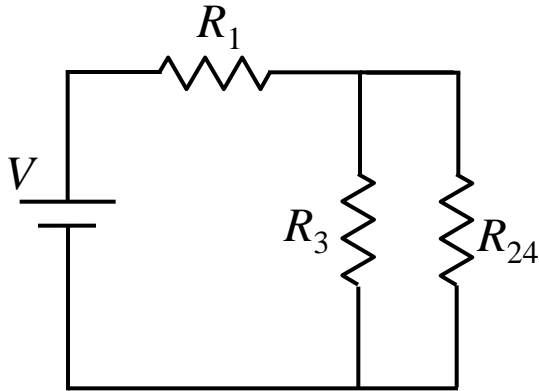

$$V = 18V$$

$$R_1 = 1\Omega$$

$$R_2 = 2\Omega$$

$$R_3 = 3\Omega$$

$$R_4 = 4\Omega.$$

$$R_{24} = 6\Omega$$

$$R_{234} = 2\Omega$$

$$I_{1234} = 6 \text{ Amps}$$

$$I_{234} = 6 \text{ Amps}$$

$$V_{234} = 12V$$

$$V_{24} = 12V$$

$$I_{24} = 2 \text{ Amps}$$

What is V_2 ?

Which of the following are true?

- A) $V_{24} = V_2$ B) $I_{24} = I_2$ C) Both A+B D) None

R_2 and R_4 where combined in series to get R_{24} → Currents are same!

Ohm's Law

$$V_2 = I_2 R_2$$

$$= 2 \times 2$$

$$= 4 \text{ Volts!}$$

The Problem Can Now Be Solved!